

Project (1): Spartan6 - DSP48A1

Ahmed Saad Sweffi

Under the Supervision of Eng. Kareem Wassem

1 RTL Code for the Design and Mux

1.1 Mux Code

```
1 module reg_mux(rst, clk, ce, sel, in, out_mux);
2     parameter reg_size = 18;
3     parameter RST_TYPE = "SYNC";
4     input rst, clk, ce, sel;
5     input [reg_size-1:0] in;
6     output wire [reg_size-1:0] out_mux;
7     reg [reg_size-1:0] out_ff;
8
9     generate
10         if (RST_TYPE == "SYNC") begin
11             always @(posedge clk) begin
12                 if (rst)
13                     out_ff <= {reg_size{1'b0}};
14                 else if (ce)
15                     out_ff <= in;
16             end
17         end else begin
18             always @(posedge clk or posedge rst) begin
19                 if (rst)
20                     out_ff <= {reg_size{1'b0}};
21                 else if (ce)
22                     out_ff <= in;
23             end
24         end
25     endgenerate
26
27     assign out_mux = (sel) ? out_ff : in;
28 endmodule
```

1.2 DSP Design Code

```
1 module firstDSP(A, B, C, D, CARRYIN, clk, opmode, BCIN,
2     CEA, CEB, CEC, CECARRYIN, CED, CEM, CEOPMODE, CEP,
3     RSTA, RSTB, RSTC, RSTCARRYIN, RSTD, RSTM, RSTOPMODE, RSTP,
4     BCOUT, PCIN, PCOUT, M, P, CARRYOUT, CARRYOUTF);
5
6     parameter A0REG = 0;
7     parameter A1REG = 1;
8     parameter B0REG = 0;
9     parameter B1REG = 1;
10    parameter CREG = 1;
11    parameter DREG = 1;
12    parameter MREG = 1;
13    parameter PREG = 1;
14    parameter CARRYINREG = 1;
15    parameter CARRYOUTREG = 1;
```

```

16 parameter OPMODEREG = 1;
17 parameter CARRYINSEL = "OPMODE5";
18 parameter B_INPUT = "DIRECT";
19 parameter RSTTYPE = "SYNC";
20
21 input clk, CEA, CEB, CEC, CECARRYIN, CED, CEM, CEOPMODE, CEP;
22 input RSTA, RSTB, RSTC, RSTCARRYIN, RSTD, RSTM, RSTOPMODE, RSTP,
    CARRYIN;
23 input [7:0] opmode;
24 input [17:0] A, B, D, BCIN;
25 input [47:0] C, PCIN;
26 output CARRYOUT, CARRYOUTF;
27 output [17:0] BCOUT;
28 output [35:0] M;
29 output [47:0] P, PCOUT;
30
31 wire CYI, CIN, carryout_postsum;
32 wire [7:0] opmode_mux;
33 wire [17:0] A0, A1, B0, B1, D_mux, B_mux, PRE_SUM, B0_mux;
34 wire [35:0] prod;
35 wire [47:0] C_mux, conc_signal, post_sum;
36 reg [47:0] X_mux, Z_mux;
37
38 assign CYI = (CARRYINSEL == "OPMODE5") ? opmode_mux[5] : (
    CARRYINSEL == "CARRYIN") ? CARRYIN : 0;
39 assign B_mux = (B_INPUT == "DIRECT") ? B : (B_INPUT == "CASCADE
    ") ? BCIN : 0;
40 assign PRE_SUM = (opmode_mux[6]) ? D_mux - B0 : D_mux + B0;
41 assign B0_mux = (opmode_mux[4]) ? PRE_SUM : B0;
42 assign conc_signal = {D_mux[11:0], A1, B1};
43 assign prod = A1 * B1;
44 assign BCOUT = B1;
45 assign {carryout_postsum, post_sum} = (opmode_mux[7]) ? (Z_mux -
    (X_mux + CIN)) : (Z_mux + X_mux + CIN);
46 assign CARRYOUTF = CARRYOUT;
47 assign PCOUT = P;
48
49 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) A0_REG (RSTA, clk,
    CEA, A0REG, A, A0);
50 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) A1_REG (RSTA, clk,
    CEA, A1REG, A0, A1);
51 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) B0_REG (RSTB, clk,
    CEB, A0REG, B_mux, B0);
52 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) B1_REG (RSTB, clk,
    CEB, A1REG, B0_mux, B1);
53 reg_mux #(.reg_size(18), .RST_TYPE(RSTTYPE)) D_REG (RSTD, clk,
    CED, DREG, D, D_mux);
54 reg_mux #(.reg_size(48), .RST_TYPE(RSTTYPE)) C_REG (RSTC, clk,
    CEC, CREG, C, C_mux);
55 reg_mux #(.reg_size(8), .RST_TYPE(RSTTYPE)) OPMODE_REG (
    RSTOPMODE, clk, CEOPMODE, OPMODEREG, opmode, opmode_mux);

```

```

56 reg_mux #(.reg_size(36), .RST_TYPE(RSTTYPE)) M_REG (RSTM, clk,
    CEM, MREG, prod, M);
57 reg_mux #(.reg_size(1), .RST_TYPE(RSTTYPE)) CARRYIN_REG (
    RSTCARRYIN, clk, CECARRYIN, CARRYINREG, CYI, CIN);
58 reg_mux #(.reg_size(1), .RST_TYPE(RSTTYPE)) CARRYOUT_REG (
    RSTCARRYOUT, clk, CECARRYOUT, CARRYOUTREG, carryout_postsum,
    CARRYOUT);
59 reg_mux #(.reg_size(48), .RST_TYPE(RSTTYPE)) P_REG (RSTP, clk,
    CEP, PREG, post_sum, P);
60
61 always @(*) begin
62     case ({opmode_mux[1], opmode_mux[0]})
63         2'b00: X_mux = 0;
64         2'b01: X_mux = M;
65         2'b10: X_mux = PCOUT;
66         2'b11: X_mux = conc_signal;
67     endcase
68 end
69
70 always @(*) begin
71     case ({opmode_mux[3], opmode_mux[2]})
72         2'b00: Z_mux = 0;
73         2'b01: Z_mux = PCIN;
74         2'b10: Z_mux = P;
75         2'b11: Z_mux = C_mux;
76     endcase
77 end
78 endmodule

```

2 Simulation on Questa Sim

2.1 TestBench

```

1 module firstDSP_tb();
2     reg clk, CEA, CEB, CEC, CECARRYIN, CED, CEM, CEOPMODE, CEP;
3     reg RSTA, RSTB, RSTC, RSTCARRYIN, RSTD, RSTM, RSTOPMODE, RSTP,
    CARRYIN;
4     reg [7:0] opmode;
5     reg [17:0] A, B, D, BCIN;
6     reg [47:0] C, PCIN;
7     wire CARRYOUT, CARRYOUTF, CARRYOUT_2, CARRYOUTF_2;
8     wire [17:0] BCOUT, BCOUT_2;
9     wire [35:0] M, M2;
10    wire [47:0] P, P_2, PCOUT, PCOUT_2;
11
12    // Instantiate the first DUT
13    firstDSP dut (
14        .A(A), .B(B), .C(C), .D(D), .CARRYIN(CARRYIN), .clk(clk), .
    opmode(opmode), .BCIN(BCIN),

```

```

15     .CEA(CEA), .CEB(CEB), .CEC(CEC), .CECARRYIN(CECARRYIN), .CED
        (CED), .CEM(CEM), .CEOPMODE(CEOPMODE), .CEP(CEP),
16     .RSTA(RSTA), .RSTB(RSTB), .RSTC(RSTC), .RSTCARRYIN(
        RSTCARRYIN), .RSTD(RSTD), .RSTM(RSTM), .RSTOPMODE(
        RSTOPMODE), .RSTP(RSTP),
17     .BCOUT(BCOUT), .PCIN(PCIN), .PCOUT(PCOUT), .M(M), .P(P), .
        CARRYOUT(CARRYOUT), .CARRYOUTF(CARRYOUTF)
18 );
19
20 // Instantiate with modified parameters
21 firstDSP #(
22     .CARRYINSEL("CARRYIN"), .B_INPUT("CASCADE"), .RSTTYPE("ASYNC
        ")
23 ) dut_2 (
24     .A(A), .B(B), .C(C), .D(D), .CARRYIN(CARRYIN), .clk(clk), .
        opmode(opmode), .BCIN(BCIN),
25     .CEA(CEA), .CEB(CEB), .CEC(CEC), .CECARRYIN(CECARRYIN), .CED
        (CED), .CEM(CEM), .CEOPMODE(CEOPMODE), .CEP(CEP),
26     .RSTA(RSTA), .RSTB(RSTB), .RSTC(RSTC), .RSTCARRYIN(
        RSTCARRYIN), .RSTD(RSTD), .RSTM(RSTM), .RSTOPMODE(
        RSTOPMODE), .RSTP(RSTP),
27     .BCOUT(BCOUT_2), .PCIN(PCIN), .PCOUT(PCOUT_2), .M(M2), .P(
        P_2), .CARRYOUT(
28     CARRYOUT_2), .CARRYOUTF(CARRYOUTF_2)
29 );
30
31 // Clock
32 initial begin
33     clk = 1;
34     forever #2 clk = ~clk;
35 end
36
37 integer i;
38 initial begin
39     // reset
40     RSTA = 1; RSTB = 1; RSTC = 1; RSTCARRYIN = 1;
41     RSTD = 1; RSTM = 1; RSTOPMODE = 1; RSTP = 1;
42     for (i = 0; i < 10; i = i + 1) begin
43         @(negedge clk);
44         A = $random; B = $random; C = $random; D = $random; BCIN
            = $random; PCIN =
45         $random; opmode = $random;
46         CARRYIN = $random; CEA = $random; CEB = $random; CEC =
            $random; CECARRYIN =
47         $random;
48         CED = $random; CEM = $random; CEP = $random; CEOPMODE =
            $random;
49         #5;
50         // Testing internal sync reset
51         if (dut.B1 != 0 || dut.A1 != 0 || dut.D_mux != 0 || dut.
            C_mux != 0 || dut.opmode_mux != 0 || dut.M != 0 || dut.CIN

```

```

    != 0 || dut.CARRYOUT != 0 || dut.P != 0) begin
$display("Error in SYNCH RESET functionality");
$stop;
end
// Testing internal async reset
if (dut_2.B1 != 0 || dut_2.A1 != 0 || dut_2.D_mux != 0 ||
    dut_2.C_mux != 0 || dut_2.opmode_mux != 0 || dut_2.M != 0
    || dut_2.CIN != 0 || dut_2.CARRYOUT != 0 || dut_2.P != 0)
    begin
$display("Error in ASYNCH RESET functionality");
$stop;
end
end
$display("RESET TEST PASSED");

// Deassert reset
RSTA = 0; RSTB = 0; RSTC = 0; RSTCARRYIN = 0;
RSTD = 0; RSTM = 0; RSTOPMODE = 0; RSTP = 0;
CEA = 0; CEB = 0; CEC = 0; CECARRYIN = 0; CED = 0; CEM = 0;
CEOPMODE = 0; CEP = 0;
for (i = 0; i < 10; i = i + 1) begin
    @(negedge clk);
    A = $random; B = $random; C = $random; D = $random; BCIN =
        $random; PCIN =
$random; opmode = $random;
    CARRYIN = $random;
    #5;
    // Testing clock enable with sync reset
    if (dut.B1 != 0 || dut.A1 != 0 || dut.D_mux != 0 || dut.
        C_mux != 0 || dut.opmode_mux != 0 || dut.M != 0 || dut.CIN
        != 0 || dut.CARRYOUT != 0 || dut.P != 0) begin
        $display("Error in CLOCK ENABLE functionality");
        $stop;
    end
    // Testing clock enable with async reset
    if (dut_2.B1 != 0 || dut_2.A1 != 0 || dut_2.D_mux != 0
        || dut_2.C_mux != 0 || dut_2.opmode_mux != 0 || dut_2.M
        != 0 || dut_2.CIN != 0 || dut_2.CARRYOUT != 0 ||
        dut_2.P != 0) begin
        $display("Error in CLOCK ENABLE functionality");
        $stop;
    end
end
end
$display("CLOCK ENABLE TEST PASSED");

// Testing specific functional cases
@(negedge clk);
CEA = 1; CEB = 1; CEC = 1; CECARRYIN = 1; CED = 1; CEM = 1;
CEOPMODE = 1; CEP = 1;
A = 1; B = 2; C = 3; D = 4; opmode = 8'b00111101; BCIN = 5;
CARRYIN = 0;

```

```

90         repeat (5) @(negedge clk);
91
92         opmode = 8'b00000011; BCIN = 10; CARRYIN = 1;
93         repeat (5) @(negedge clk);
94
95         opmode = 8'b10011010; BCIN = 5; CARRYIN = 0;
96         repeat (5) @(negedge clk);
97
98         opmode = 8'b10100101; BCIN = 10; CARRYIN = 0; PCIN = 100;
99         repeat (10) @(negedge clk);
100
101         $stop;
102     end
103 endmodule

```

2.2 Do File

```

1 vsim -voptargs=+acc work.firstDSP_tb
2 add wave-position insertpoint \
3 sim:/firstDSP_tb/clk \
4 sim:/firstDSP_tb/CEA \
5 sim:/firstDSP_tb/CEB \
6 sim:/firstDSP_tb/CEC \
7 sim:/firstDSP_tb/CECARRYIN \
8 sim:/firstDSP_tb/CED \
9 sim:/firstDSP_tb/CEM \
10 sim:/firstDSP_tb/CEOPMODE \
11 sim:/firstDSP_tb/CEP \
12 sim:/firstDSP_tb/RSTA \
13 sim:/firstDSP_tb/RSTB \
14 sim:/firstDSP_tb/RSTC \
15 sim:/firstDSP_tb/RSTCARRYIN \
16 sim:/firstDSP_tb/RSTD \
17 sim:/firstDSP_tb/RSTM \
18 sim:/firstDSP_tb/RSTOPMODE \
19 sim:/firstDSP_tb/RSTP \
20 sim:/firstDSP_tb/CARRYIN \
21 sim:/firstDSP_tb/opmode \
22 sim:/firstDSP_tb/A \
23 sim:/firstDSP_tb/B \
24 sim:/firstDSP_tb/D \
25 sim:/firstDSP_tb/BCIN \
26 sim:/firstDSP_tb/C \
27 sim:/firstDSP_tb/PCIN \
28 sim:/firstDSP_tb/CARRYOUT \
29 sim:/firstDSP_tb/CARRYOUTF \
30 sim:/firstDSP_tb/CARRYOUT_2 \
31 sim:/firstDSP_tb/CARRYOUTF_2 \
32 sim:/firstDSP_tb/BCOUT \
33 sim:/firstDSP_tb/BCOUT_2 \

```

```

34 sim:/firstDSP_tb/M \
35 sim:/firstDSP_tb/M2 \
36 sim:/firstDSP_tb/P \
37 sim:/firstDSP_tb/P_2 \
38 sim:/firstDSP_tb/PCOUT \
39 sim:/firstDSP_tb/PCOUT_2 \
40 sim:/firstDSP_tb/i
41 run -all

```

3 Design Figures


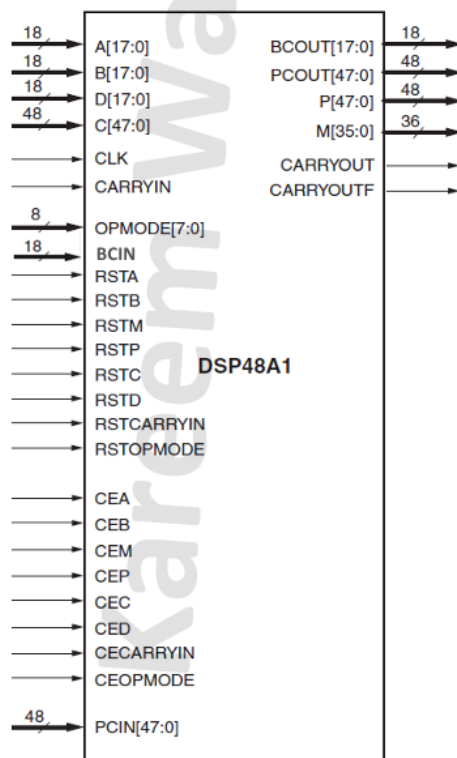


Figure 1: The DSP4A1.

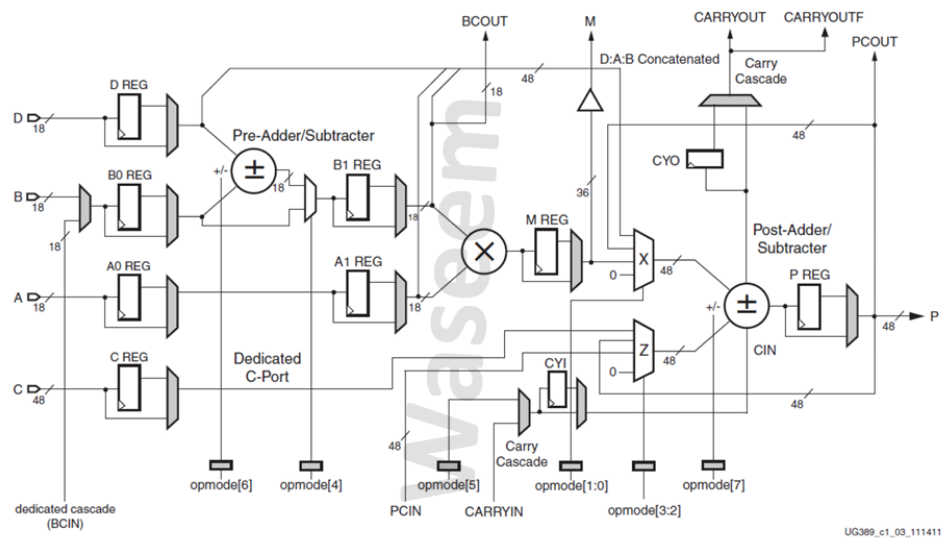

Note: opmode input has a register and mux pair in the design entry the same way as the input A, D, or C

Figure 2: The Elaborated Design.

```

# RESET TEST PASSED
# CLOCK ENABLE TEST PASSED
# ** Note: $stop : C:/Users/ahmed saad/Downloads/project 1/DSP_tb.v(101)
# Time: 262 ns Iteration: 1 Instance: /firstDSP_tb
# Break in Module firstDSP_tb at C:/Users/ahmed saad/Downloads/project 1/DSP_tb.v line 101
VSIM 6>

```

Figure 3: The messages bar shows no critical errors.

 


Figure 4: Wave form.

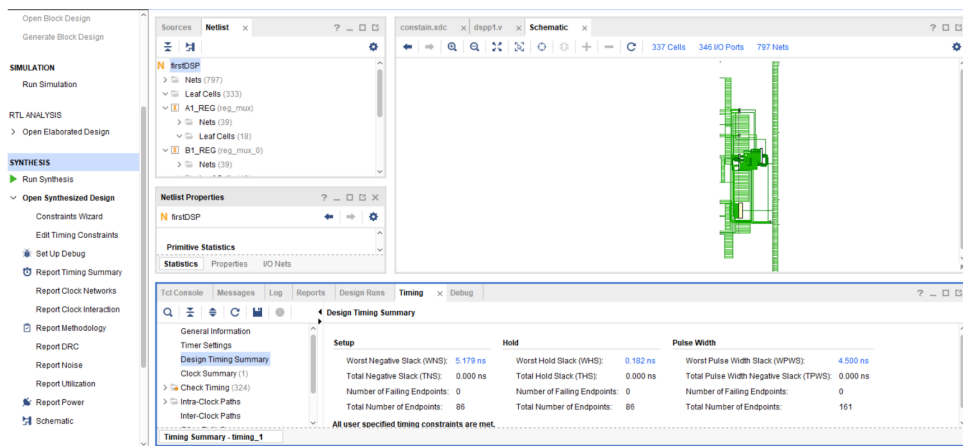


Figure 5: Report Timing Summary.

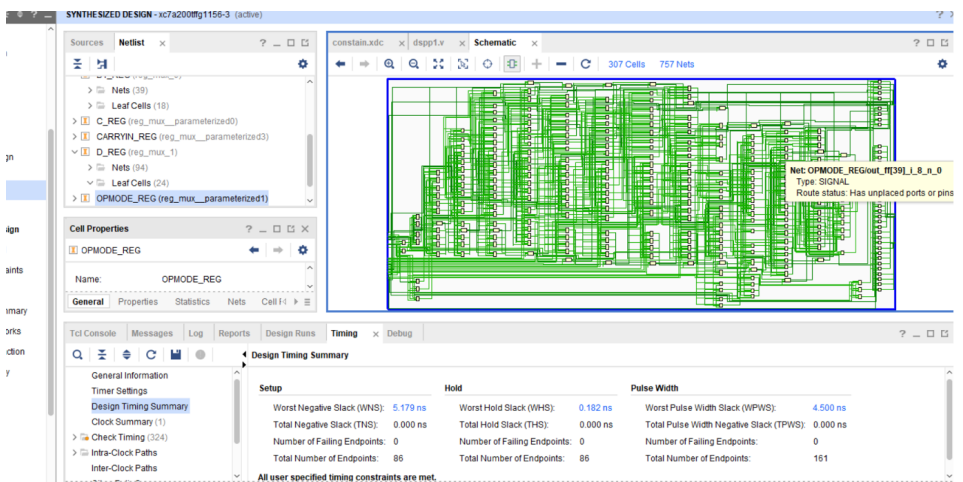


Figure 6: Inside the design of the Opmode.

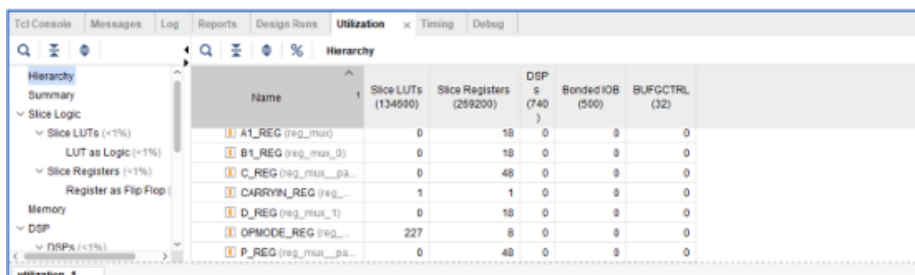


Figure 7: Utilization Report.

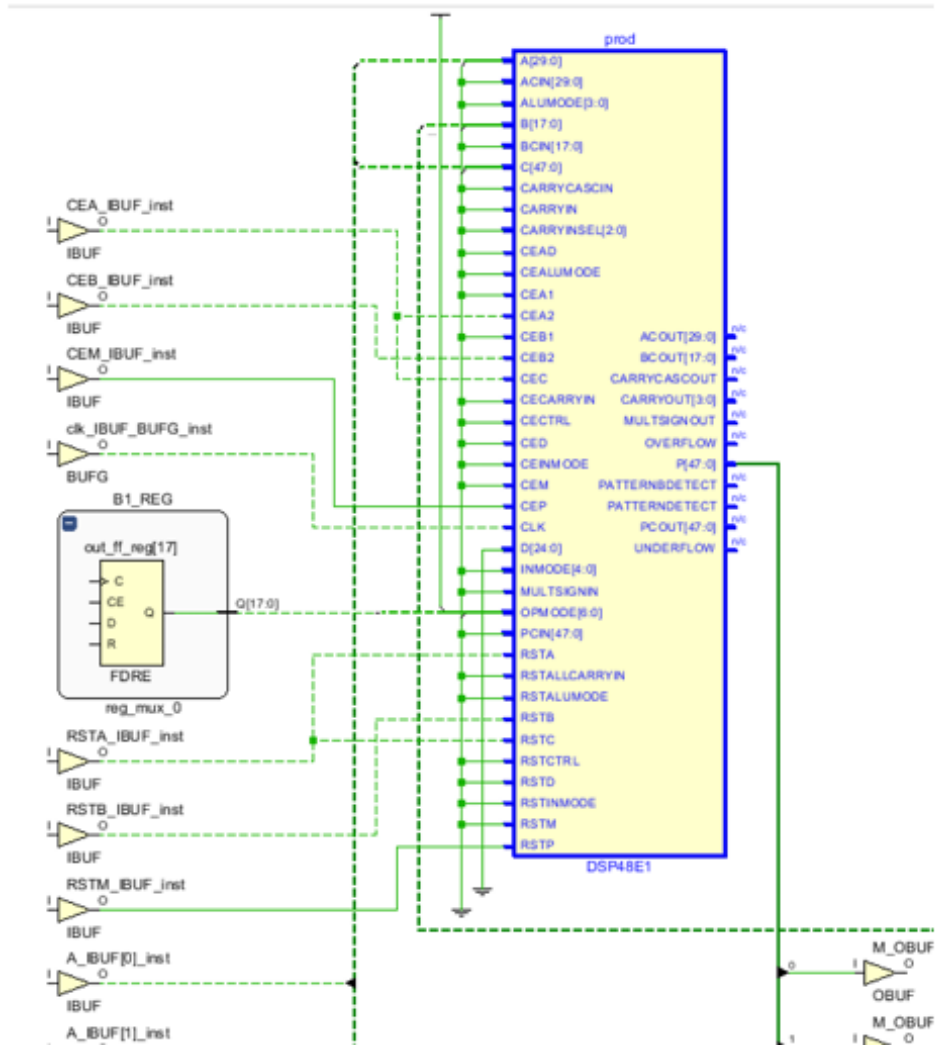


Figure 8: The DSP4A1.

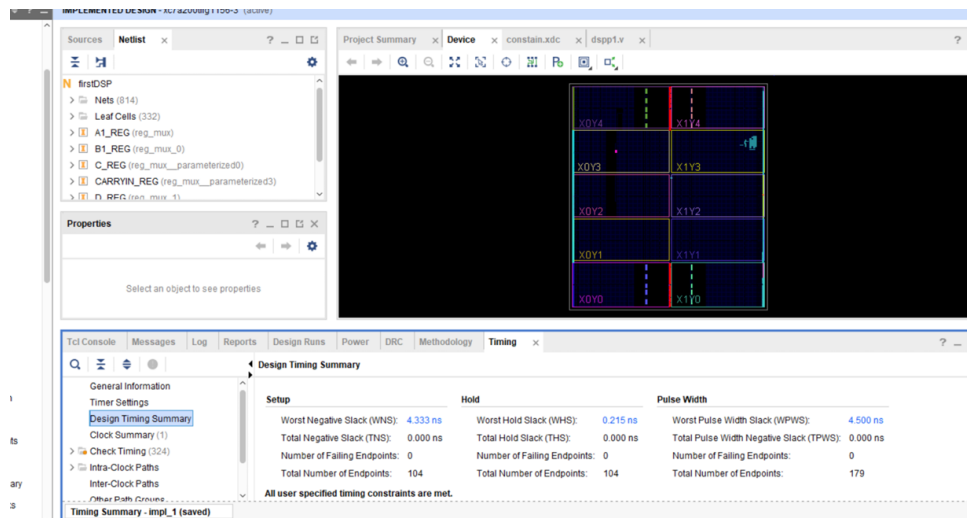


Figure 9: The Implementation Design after running it.

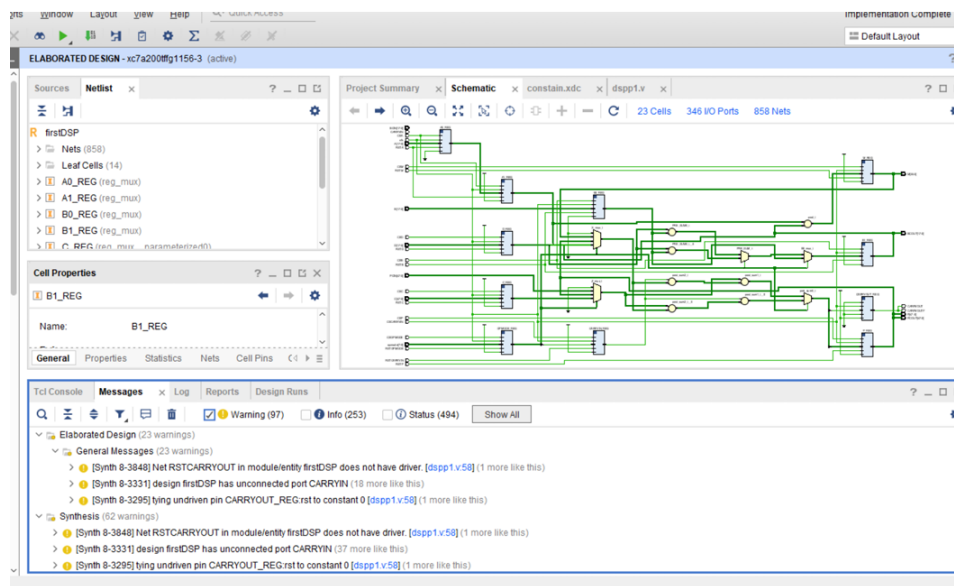


Figure 10: The Elaborated Design and messages.

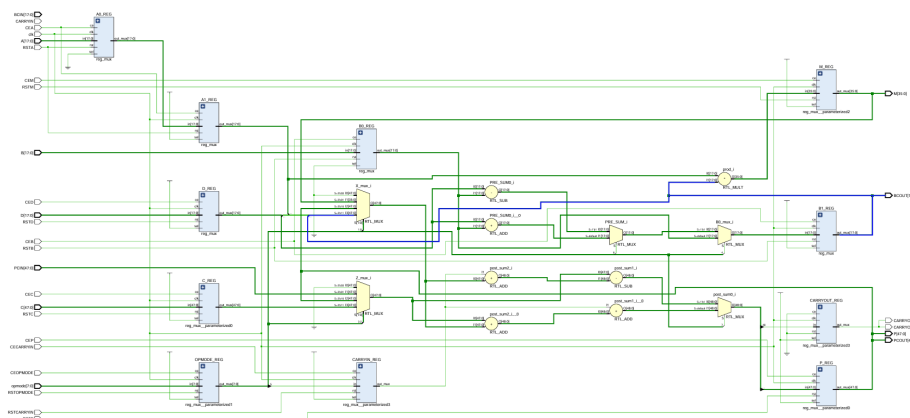


Figure 11: The Elaborated Design.